
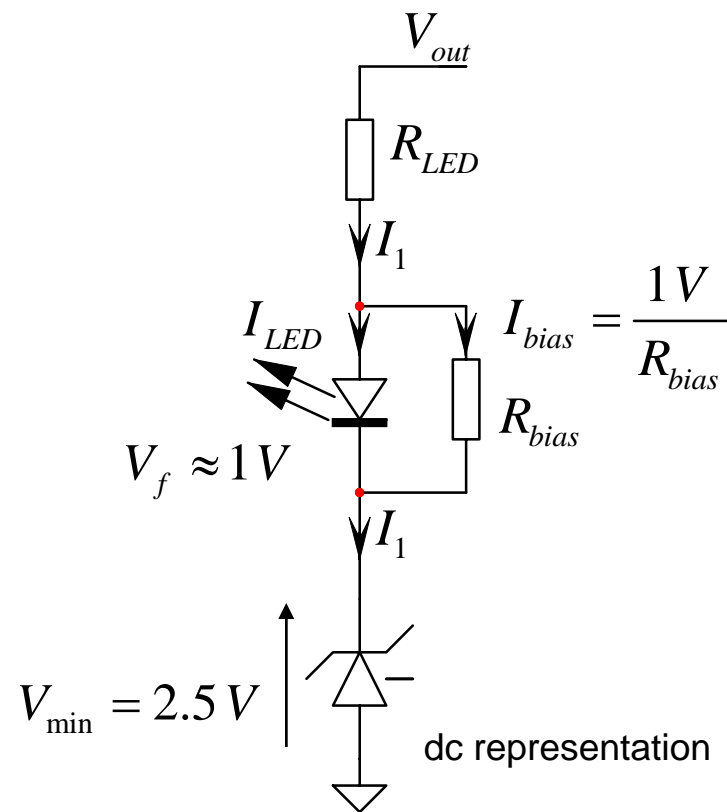


The TL431 Programmable Zener

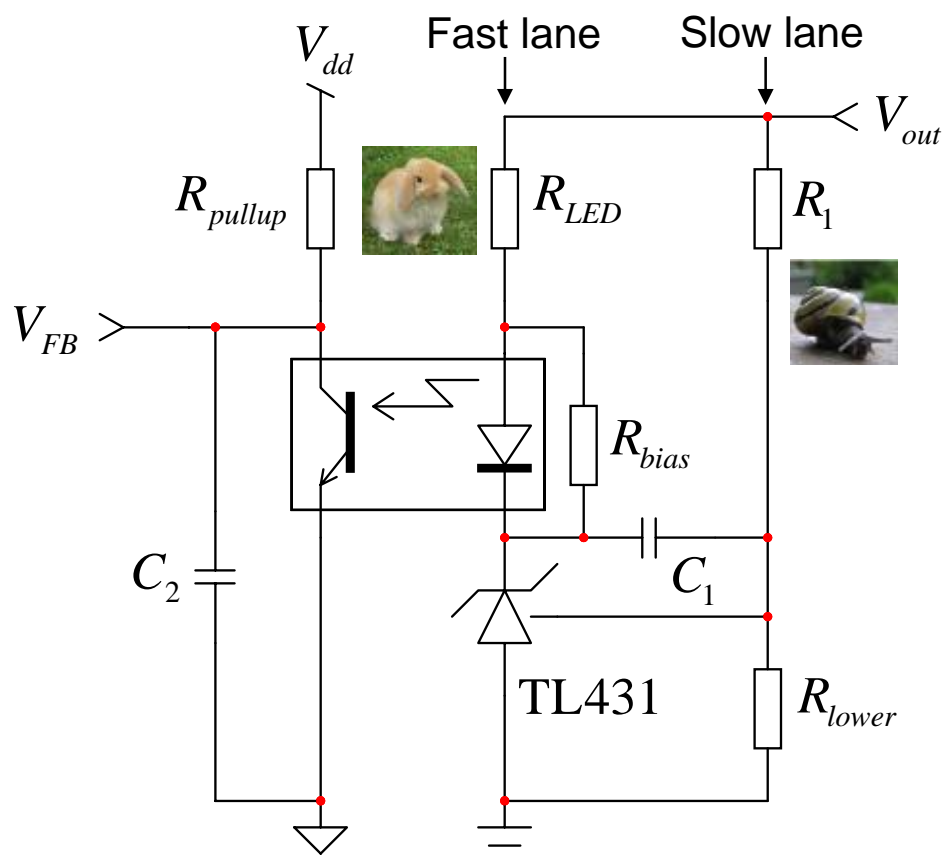- The TL431 lends itself very well to optocoupler control




- R_{LED} must leave enough headroom over the TL431: upper limit!

The TL431 Programmable Zener

- This LED resistor is a design limiting factor in low output voltages:

$$R_{LED,max} \leq \frac{V_{out} - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min}$$

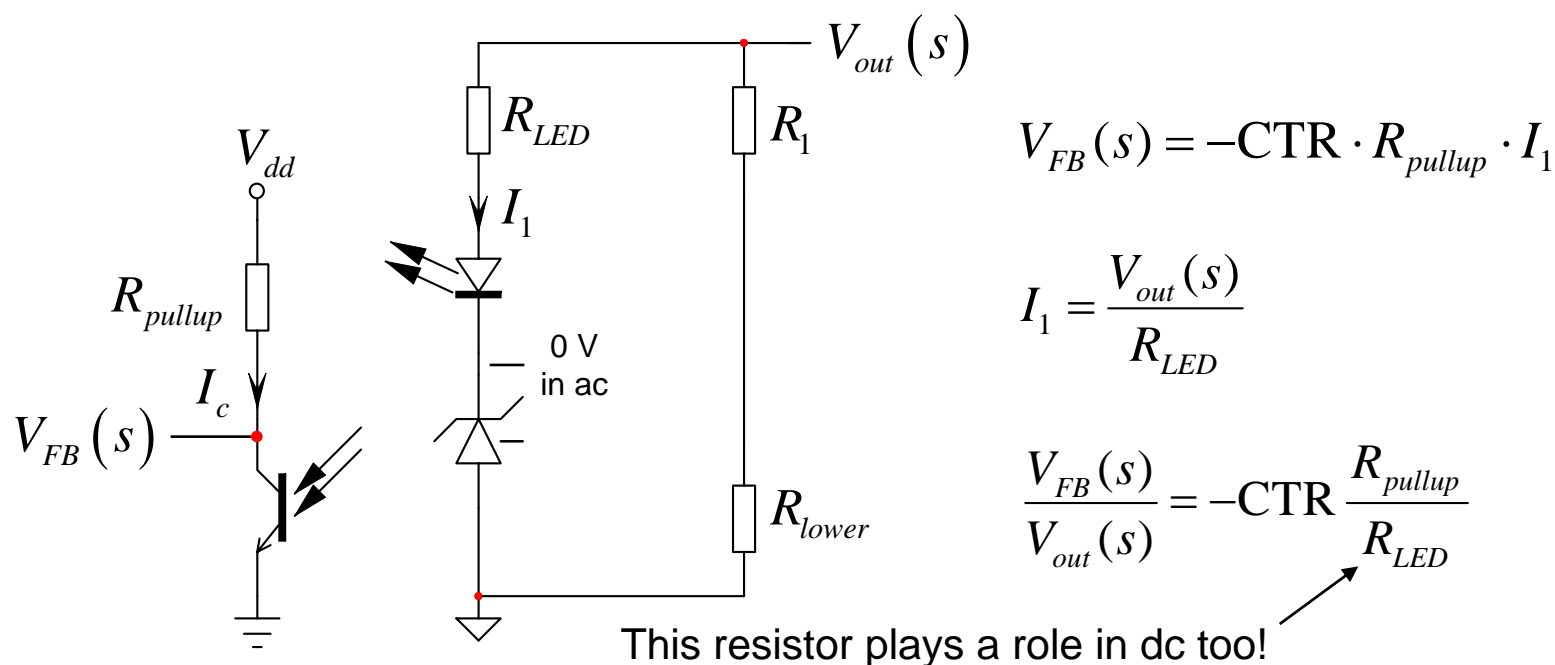- When the capacitor C_1 is a short-circuit, R_{LED} fixes the fast lane gain



$$V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$$

$$I_1 = \frac{V_{out}(s)}{R_{LED}}$$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -CTR \frac{R_{pullup}}{R_{LED}}$$

The TL431 – the Static Gain Limit

- Let us assume the following design:

$$V_{out} = 5 V$$

$$V_f = 1 V$$

$$V_{TL431,min} = 2.5 V$$

$$V_{dd} = 4.8 V$$


$$V_{CE,sat} = 300 mV$$

$$I_{bias} = 1 mA$$

$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 k\Omega$$
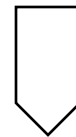
$$R_{LED,max} \leq \frac{5 - 1 - 2.5}{4.8 - 0.3 + 1m \times 0.3 \times 20k} \times 20k \times 0.3$$



$$R_{LED,max} \leq 857 \Omega$$



$$G_0 > CTR \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{0.857} > 7 \text{ or } \approx 17 \text{ dB}$$

- In designs where R_{LED} fixes the gain, G_0 cannot be below 17 dB

⇒ You cannot “amplify” by less than 17 dB