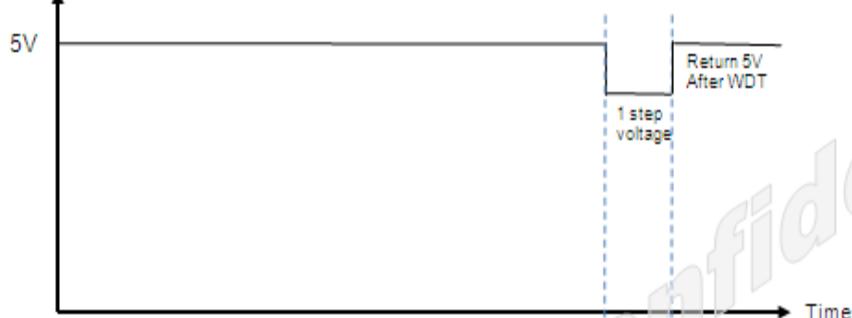


Output  
Voltage

### Decrease Output Voltage



Output  
current


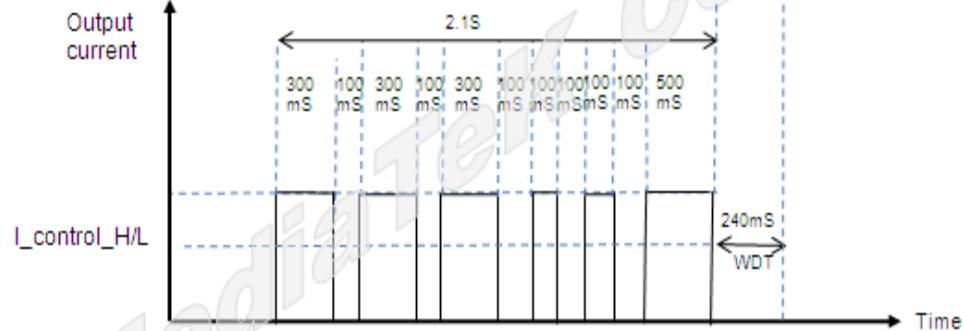


Fig 3a. Current control, decrease output voltage

### Increase Output Voltage

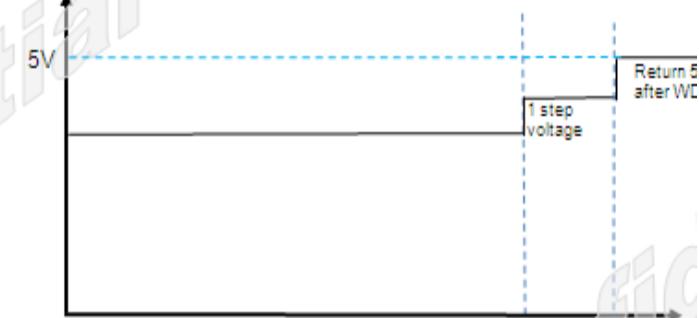

I\_control\_H/L

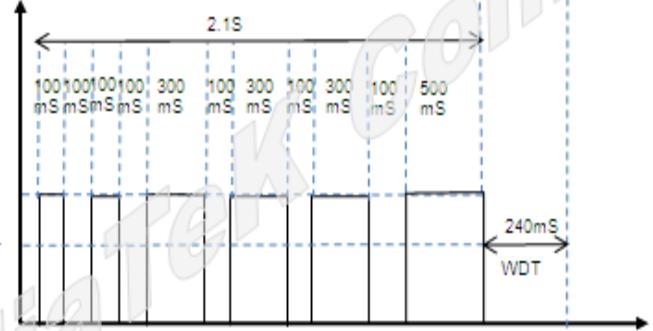


Fig 3b. Current control, increase output voltage