



1000W不对称半桥LLC谐振电源参数计算书



客户需求：

输入参数：
占空比 $D := 0.5$ 效率 $\eta := 0.94$
输入电压 $V_{in_min} := 390V$ $V_{in_max} := 410V$ $V_{in_nor} := 400V$

输出参数：
输出电压 $V_{out} := 24V$ $V_{out_pk} := V_{out} \cdot 0.01 = 0.24V$
输出电流 $I_{out} := 41.7A$
整流二极管压降 $V_d := 0.7V$
输出功率 $P_{out} := V_{out} \cdot I_{out} = 1.001 \times 10^3 W$
过流保护 $O_{cp} := 1.3$

预设参数：
谐振频率 $f_r := 100kHz$
电感比 $k := 6$
MOS管输出电容 $C_{oss} := 80pF$ $C_{stray} := 200pF$
死区时间 $T_d := 300ns$



谐振参数



输出最大电流 $I_{out_max} := I_{out} \cdot 1.2 = 50.04 A$

输出最小电流 $I_{out_min} := I_{out} \cdot 0.001 = 0.042 A$

额定输入功率 $P_{in_nor} := \frac{P_{out}}{\eta} = 1.065 \times 10^3 W$

变压器匝比 $n := \frac{V_{in_nor}}{2 \cdot (V_{out} + V_d)} = 8.097$

最大增益 $G_{max} := 2 \cdot n \cdot \frac{V_{out} + V_d}{V_{in_min}} = 1.026$

最小增益 $G_{min} := 2 \cdot n \cdot \frac{V_{out} + V_d}{V_{in_max}} = 0.976$

峰值增益 $G_{max_pk} := G_{max} \cdot 1.15 = 1.179$

额定负载电阻 $R_o := \frac{V_{out}}{I_{out}} = 0.576 \Omega$

最小负载电阻 $R_o_{min} := \frac{V_{out}}{I_{out_max}} = 0.48 \Omega$

最大负载电阻 $R_{o_max} := \frac{V_{out}}{I_{out_min}} = 575.54 \Omega$

等效交流电阻 $R_{ac} := \frac{8 \cdot n^2 \cdot R_o}{\pi^2} = 30.587 \Omega$

最小交流电阻 $R_{ac_min} := \frac{8 \cdot n^2 \cdot R_{o_min}}{\pi^2} = 25.489 \Omega$


最大交流电阻 $R_{ac_max} := \frac{8 \cdot n^2 \cdot R_{o_max}}{\pi^2} = 3.059 \times 10^4 \Omega$


直流增益 $M(x, k, Q) := \frac{1}{\sqrt{\left[1 + \frac{1}{k} \cdot \left(1 - \frac{1}{x^2}\right)\right]^2 + \left(x - \frac{1}{x}\right)^2 Q^2}}$

阻性增益 $M_r(x, k) := \frac{1}{\sqrt{\left[1 + \frac{1}{k} \cdot \left(1 - \frac{1}{x^2}\right)\right]^2 + \left(x - \frac{1}{x}\right)^2 \left[\frac{1}{k(1-x^2)} - \frac{1}{(k \cdot x)^2}\right]}}$

$$Q = \frac{2\pi f_r L_r}{R_{ac}} \quad Z = \frac{Z_{in}}{R_{ac} Q} = \frac{Z_{in}}{2\pi f_r L_r}$$

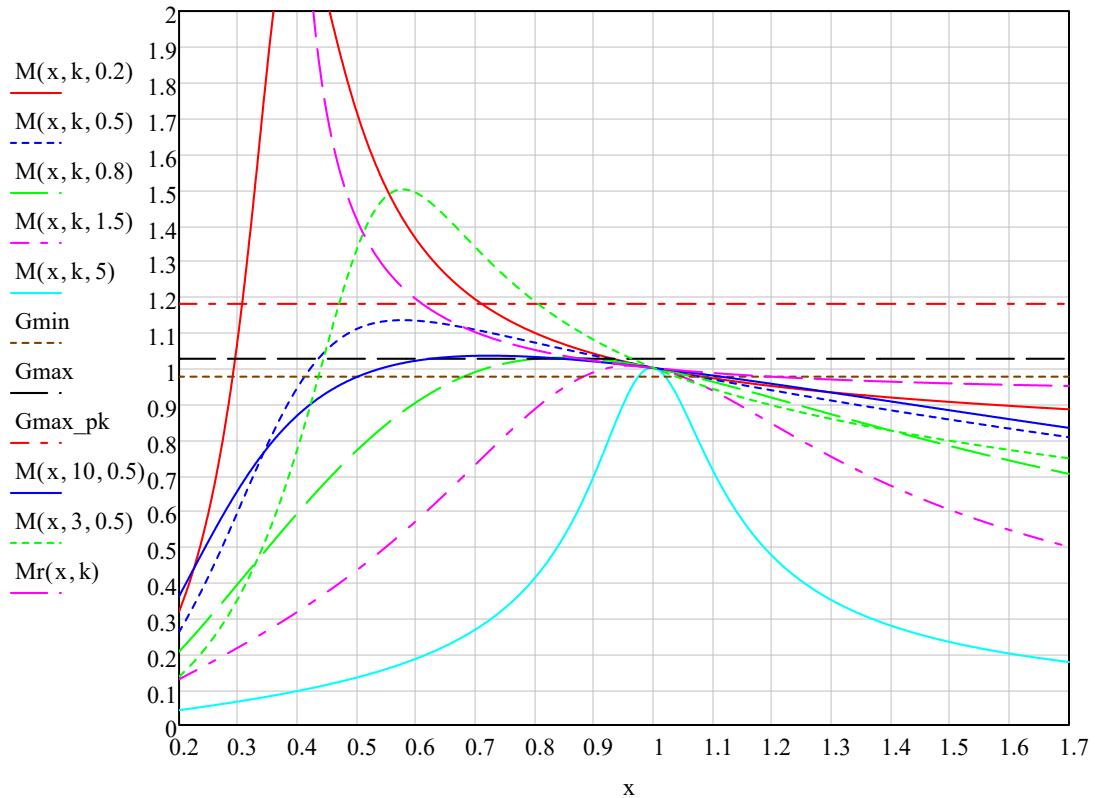阻抗 $Z(x, k, Q) := \sqrt{\left(\frac{k^2 \cdot x^2 Q}{1 + x^2 \cdot k^2 \cdot Q^2}\right)^2 + \left[x - \frac{1}{x} + \frac{x \cdot k}{1 + (k \cdot Q \cdot x)^2}\right]^2}$



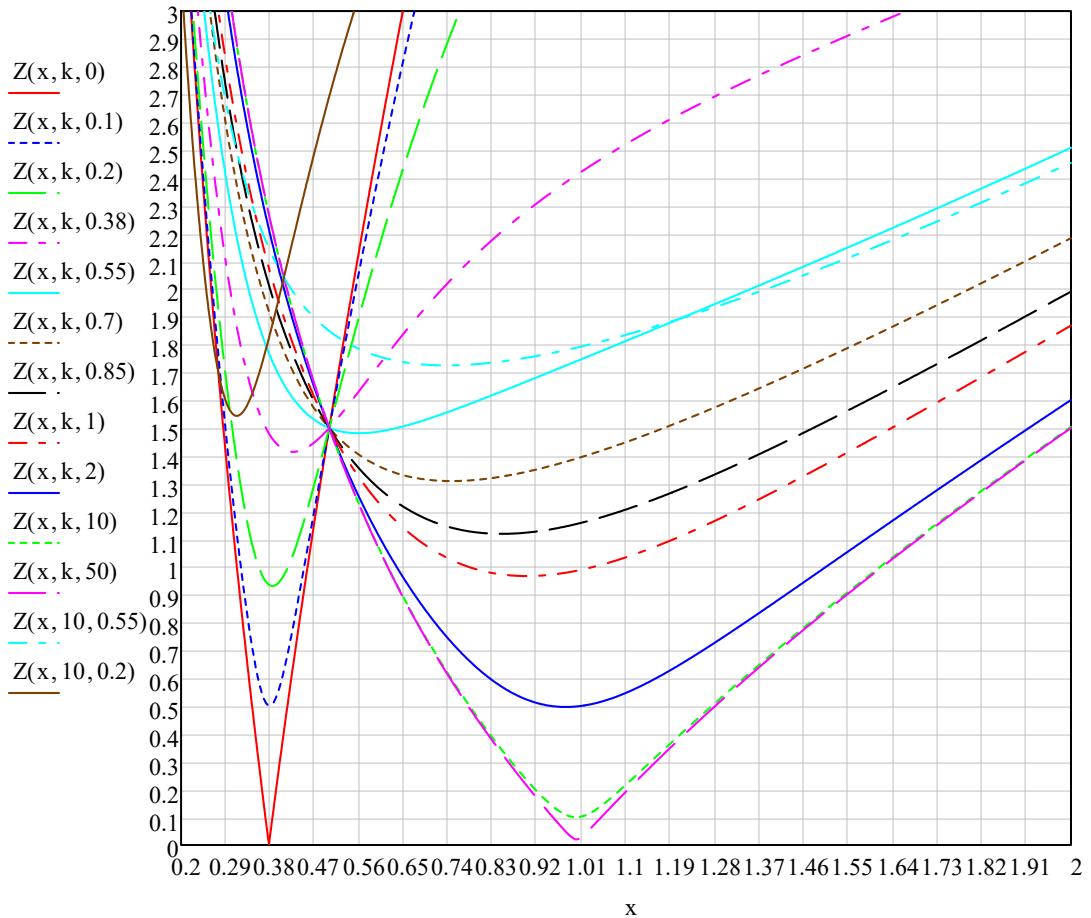

最小开关频率 $f_{min} := \frac{fr}{\sqrt{1 + k \cdot \left(1 - \frac{1}{G_{max}^2}\right)}} = 8.783 \times 10^4 \text{ Hz}$

最大开关频率 $f_{max} := \frac{fr}{\sqrt{1 + k \cdot \left(1 - \frac{1}{G_{min}}\right)}} = 1.085 \times 10^5 \text{ Hz}$

最大负载

$$Q_{\max} := \frac{1}{k \cdot G_{\max}} \cdot \sqrt{k + \frac{G_{\max}^2}{G_{\max}^2 - 1}} = 0.833$$

谐振电容

$$C_R := \frac{1}{2 \cdot \pi \cdot f_R \cdot R_{AC_min} \cdot Q_{\max}} = 7.499 \times 10^{-8} F$$

谐振电感

$$L_R := \frac{Q_{\max} \cdot R_{AC_min}}{2 \cdot \pi \cdot f_R} = 3.378 \times 10^{-5} H$$

励磁电感

$$L_M := k \cdot L_R = 2.027 \times 10^{-4} H$$

谐振电流有效值

$$I_{LR_rms} := \frac{V_{out}}{8 \cdot n \cdot R_{o_min}} \cdot \sqrt{\frac{2 \cdot n^4 \cdot R_{o_min}^2}{L_M^2 \cdot f_R^2}} = 7.07 A$$

谐振电流峰值

$$I_{LR_pk} := \sqrt{2} \cdot I_{LR_rms} = 9.999 A$$

谐振电容电压峰值

$$V_{CR_pk} := \frac{V_{in_max}}{2} + \frac{I_{LR_pk}}{2 \cdot \pi \cdot f_{min} \cdot C_R} = 446.6 V$$

ZVS验证 $I_{LM_min} > I_p$ 电容的充电电流小于放电电流

$$I_{LM_min} := \frac{V_{in_max}}{L_M} \cdot \frac{1}{4 \cdot f_{max}} = 4.663 A$$

电容充电电流

$$I_p := (2 \cdot C_{oss} + C_{stray}) \cdot \frac{V_{in_nor}}{T_d} = 0.48 A \quad \text{满足ZVS}$$

MOS管应力

$$I_{mos} := 3 \cdot I_{LR_pk} = 29.997 A \quad V_{mos} := \frac{V_{in_max}}{0.7} = 585.714 V$$

整流二极管应力

$$I_{dd} := 3 \cdot \frac{\pi \cdot I_{out_max}}{4} = 117.904 A \quad V_{dd} := \frac{2(V_{out} + V_d)}{0.7} = 70.571 V$$

输出电流纹波

$$I_{Co} := \sqrt{\frac{\pi^2 - 8}{8}} \cdot I_{out_max} = 24.191 A$$

等效电阻ESR

$$ESR := \frac{V_{out_pk}}{0.5 \cdot \pi \cdot I_{out_max}} = 3.053 \times 10^{-3} \Omega$$

