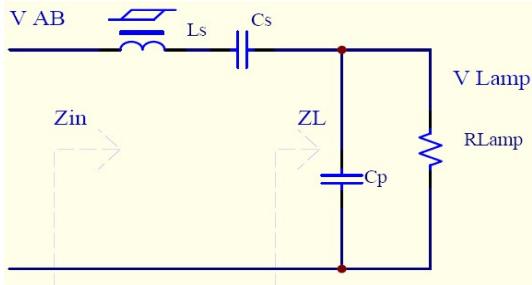


燈管 R-G 值推導



$$\text{電路增益為 } \frac{V_{\text{Lamp}}}{V_{\text{AB}}} = \frac{Z_L}{Z_{\text{in}}}$$

$$Z_L = \frac{\frac{R_{\text{Lamp}}}{j\omega_s C_p}}{R_{\text{Lamp}} + \frac{1}{j\omega_s C_p}} = \frac{R_{\text{Lamp}}}{1 + j\omega_s C_p R_{\text{Lamp}}}$$

$$\begin{aligned} Z_{\text{in}} &= \frac{1}{j\omega_s C_s} + j\omega_s L_s + \frac{R_{\text{Lamp}}}{1 + j\omega_s C_p R_{\text{Lamp}}} \\ &= \frac{(1 + j\omega_s C_p R_{\text{Lamp}}) + j\omega_s L_s [j\omega_s C_s (1 + j\omega_s C_p R_{\text{Lamp}})] + j\omega_s C_s R_{\text{Lamp}}}{j\omega_s C_s * (1 + j\omega_s C_p R_{\text{Lamp}})} \end{aligned}$$

$$\frac{V_{\text{Lamp}}}{V_{\text{AB}}} = M = \frac{\frac{R_{\text{Lamp}}}{1 + j\omega_s C_p R_{\text{Lamp}}}}{\frac{(1 + j\omega_s C_p R_{\text{Lamp}}) + j\omega_s L_s [j\omega_s C_s (1 + j\omega_s C_p R_{\text{Lamp}})] + j\omega_s C_s R_{\text{Lamp}}}{j\omega_s C_s (1 + j\omega_s C_p R_{\text{Lamp}})}}$$

從 Z_L 看進去則 $C_s \gg C_p$ 且 $C_s = nC_p$

$$M = \frac{1}{(1 + \frac{C_p}{nC_p} - \omega_s^2 L_s C_p) + j(\frac{\omega_s L_s}{R_{\text{Lamp}}} - \frac{1}{\omega_s nC_p R_{\text{Lamp}}})}$$

$$\text{設諧振頻率剛好為 } \omega_o = \frac{1}{\sqrt{L_s C_p}} , Q = \frac{R_{\text{Lamp}}}{\sqrt{L_s C_p}} , Z_o = \sqrt{\frac{L_s}{C_p}} = 2\pi f_o L_s = \frac{1}{2\pi f_o C_p} \text{ 則}$$

$$|M| = \frac{1}{[1 + \frac{1}{n} - (\frac{\omega_s}{\omega_o})^2]^2 + \frac{1}{Q^2} (\frac{\omega_s}{\omega_o} - \frac{\omega_o}{n\omega_s})^2} , \text{ 設 } x = \frac{\omega_s}{\omega_o}$$

$$|M| = \frac{1}{[1 + \frac{1}{n} - (x)^2]^2 + \frac{1}{Q^2} (x - \frac{1}{n*x})^2}$$